

Third Semester B. E. (Elect. Engg./Elec. and Power) (CGS) Examination

**ELECTRONIC DEVICES AND CIRCUITS**

Paper – 3 EP 04/3 EX 04/3 EL 04/3 EE 04

( USC – 10480 )

P. Pages : 3

Time : Three Hours ]

[Max. Marks : 80

- Note :** (1) Separate answer book must be used for each section in the subject Geology, Engineering material of Civil branch and separate answer book must be used for Section A and B in pharmacy and Cosmetic Tech.
- (2) Answer **Three** questions from Section A and **Three** questions from Section B.
- (3) Due credit will be given to neatness and adequate dimensions.
- (4) Assume suitable data wherever necessary.
- (5) Diagrams and chemical equations should be given wherever necessary.
- (6) Illustrate your answer wherever necessary with the help of neat sketches.
- (7) Use pen of Blue/Black ink/refill only for writing the answer book.

**SECTION A**

1. (a) Explain the working of PN junction diode with its characteristics. 7
- (b) What do you mean by Rectifier ? Explain Halfwave rectifier in detail. 7

**OR**

2. (a) What are different type of filter ? Explain working of capacitor input filter with proper waveforms. 7
- (b) Give expressions for TUF and Ripple factor of full wave Rectifier. 7
3. (a) Explain the amplification action in Bipolar Junction Transistor. 6
- (b) What is Bias stabilization ? Prove that

$$S = \frac{1 + \beta}{1 - \beta \left( \frac{d\beta}{dI_C} \right)}$$


7

OR

4. (a) Explain the working of NPN transistor with its input output characteristics. 7

- (b) For the following circuit  $\beta = 100$ .  
Determine

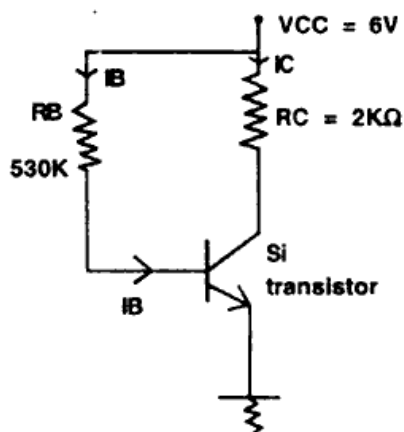- (i) Operating point  
(ii) Stability factor.



6

5. (a) Explain Bootstrapped emitter follower with circuit diagram. How input impedance increases in it ? 7  
(b) Explain with proper circuit diagram cascaded amplifier. 6

OR

6. (a) What is RC coupled amplifier ? Explain its frequency response. 7  
(b) Explain Emitter follower circuit. What are the techniques to increase its input impedance. 6

### SECTION B

7. (a) How power amplifiers are classified. Explain with suitable diagrams. 8  
(b) What is Wein bridge oscillator ? How is Barkhausen criteria satisfied there ? 6

**OR**

8. (a) Explain transformer coupled class A power amplifier. How is impedance matching occurs there ? 7
- (b) What is LC tank circuit ? Explain any one LC oscillator in detail. 7
9. (a) Explain the working of light emitting diode with its construction and characteristics. 6
- (b) Explain Tunneling phenomenon in Tunnel diode with the help of Energy band diagrams. <http://www.sgbauonline.com> 8

**OR**

10. (a) Explain with neat diagrams working of PIN diode in detail. 7
- (b) Explain the characteristics of Tunnel diode with various regions in it. 7
11. (a) Explain n – channel Enhancement type MOSFET on the basis of construction operation and characteristics. 7
- (b) Explain UJT as a relaxation oscillator. 6

**OR**

12. (a) Explain the following with reference to JFET.

(i) Drain Resistance ( $r_d$ )

(ii) Transconductance ( $g_m$ )

(iii) Amplification factor ( $\mu$ )

Also prove that  $\mu = r_d \times g_m$ . 8

- (b) Prove that

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right) \quad 5$$

