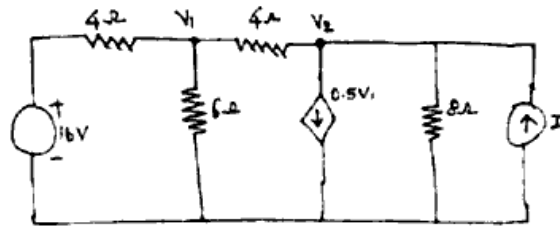





- Notes :
1. Answer **three** question from Section A and **three** question from Section B.
 2. Due credit will be given to neatness and adequate dimensions.
 3. Assume suitable data wherever necessary.
 4. Use of pen Blue/Black ink/refill only for writing the answer book.

SECTION - A

1. a) Using nodal analysis, find the value of current I to reduce the node voltage V_2 to zero. 7




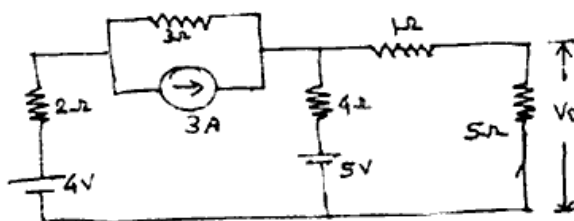- b) For the circuit shown in figure below, find V_0 & $I_{3\Omega}$. 6




OR

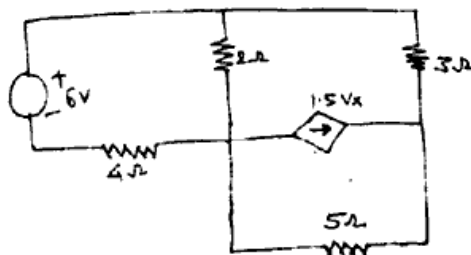2. a) Explain Dependent sources & Independent sources. 6
 b) Calculate output of current source. 7



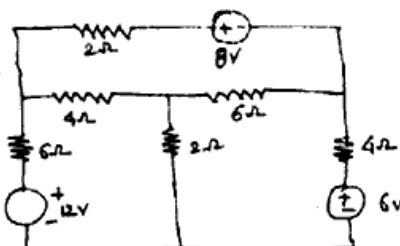3. a) A network has been shown in figure below. Write down the tie-set matrix & obtain network equilibrium equation in matrix form using KVL. 7




http://www.sgbauonline.com

http://www.sgbauonline.com

b) For the network shown below find the dual network.


6

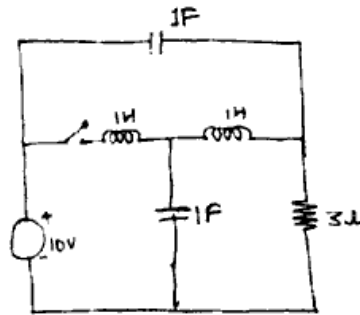

OR

4. a) For the network shown below, draw the oriented graph. Define any one tree & mention its twigs & links. Obtain incidence matrix.

7

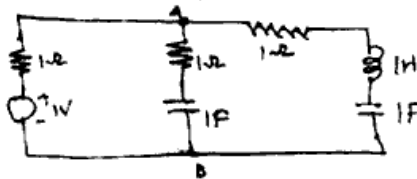


b) Obtain the full incidence matrix from the reduced incidence matrix gives below & form the oriented graph.

6

$$A = \begin{bmatrix} 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 1 \\ 1 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

5. a) For the circuit shown in figure, find the power loss in R_L using Thevenin's theorem.

7

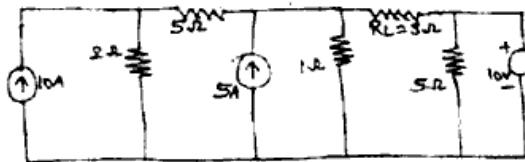


b) State and explain Millman's theorem in detail. Enumerate its limitations.

7

OR


6. a) Find the voltage across the terminals 'a - b' & verify reciprocity theorem for the circuit.

7

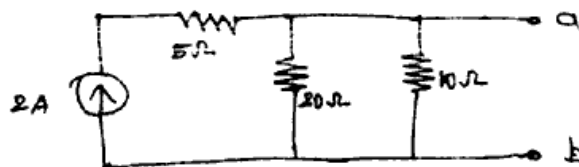


b) Find ' V_{xy} ' & ' I_{xy} ' for circuit shown below, & substitute the branch faithfully.

7

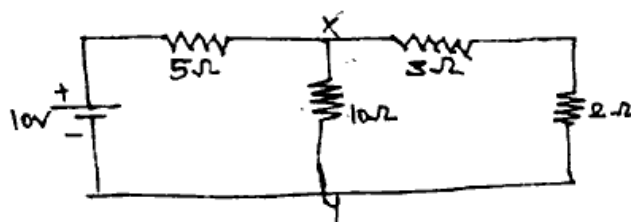


SECTION - B

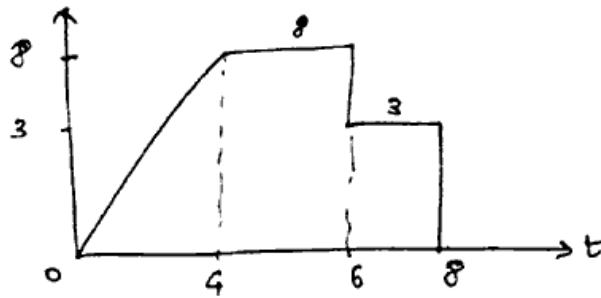7. a) Find the Laplace transform of the given figure. 7



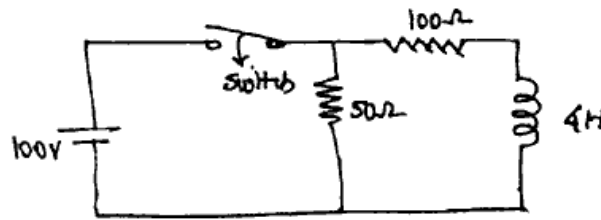
- b) If the circuit initial current 'I' is zero, find the source current after closing of switch 'S': 7




OR

8. a) Derive an expression for DC response of an R - C circuit. 7

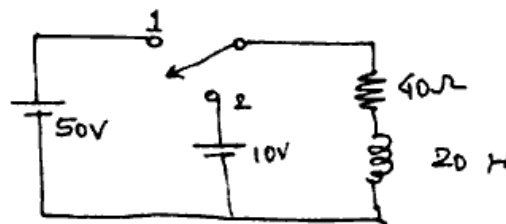
- b) The switch in figure shown below has been in position 1 for a long time, it is moved to position 2 at $t = 0$, obtain the expression for current for $t > 0$. 7



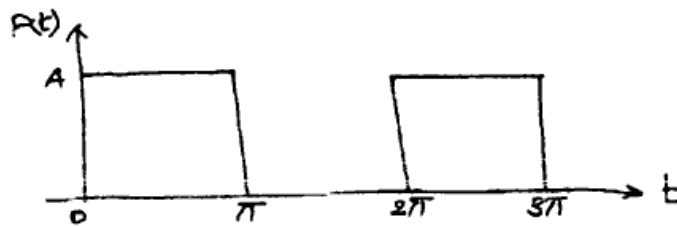9. a) Find the Fourier Series of waveform, draw the magnitude spectrum. 6




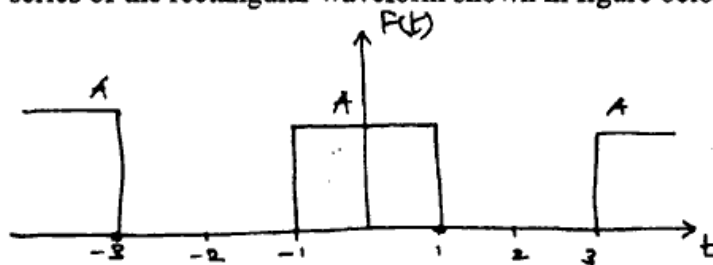- b) Find the Fourier series of the rectangular waveform shown in figure below. 7




OR

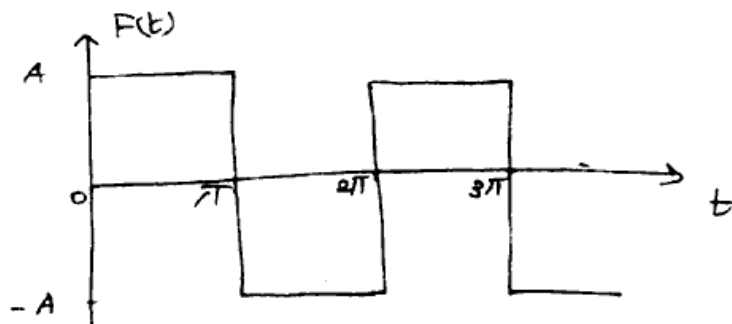10. a) Determine Fourier coefficient's for Even Symmetry. 6
 b) Find the exponential Fourier Series of waveform shown in figure below. Draw the magnitude spectrum. 7




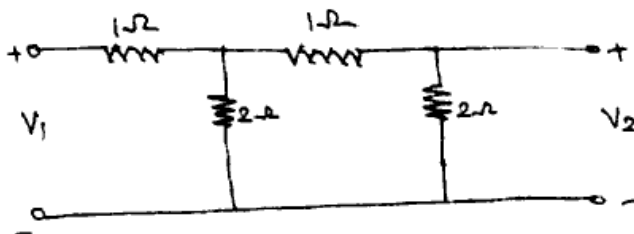11. a) Derive an expression for condition of symmetry for y - parameter. 7
 b) Find Z - parameter for the network shown below. 6



OR

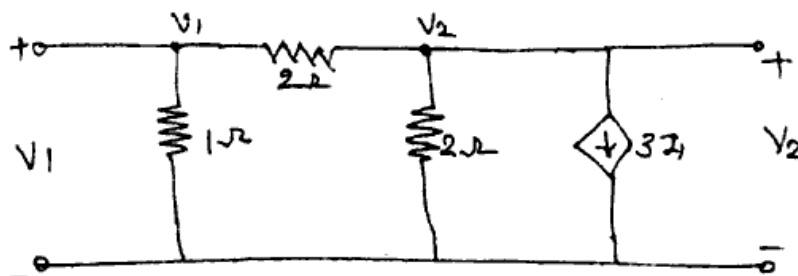12. a) Determine Y & Z parameter for the network shown in figure below. 7



- b) Determine hybrid parameter for the network shown below. 6

