

M.Sc. (First Year) Semester—II (CBCS Scheme) Examination

2-ELE-1 : ELECTRONICS

(Analog Circuit Design and Analysis)

Time : Three Hours]

[Maximum Marks : 80

- Note :—** (1) All questions carry equal marks.
(2) Draw neat diagram wherever necessary.
(3) Due credit will be given to neatness.

1. (A) Draw the block diagram of Op-Amp and explain the operation of each block. 8
(B) Discuss the following parameters of Op-Amp :
(i) Input bias current
(ii) Input bias voltage
(iii) Slew rate
(iv) CMRR. 8

OR

- (P) Draw the diagram of difference amplifier and explain its operation. Also explain A_c , A_d and CMRR. 8
(Q) Discuss the parameters of ideal Op-Amp. 8
2. (A) Draw the block diagram of amplifier with various feedback and explain the operation of voltage series feedback amplifier using Op-Amp. 8
(B) Explain the parameters in difference amplifier :
(i) Output Resistance
(ii) Bandwidth. 8

OR

- (P) Explain the operation of voltage shunt feedback amplifier using Op-Amp. 8
(Q) What is effect of feedback in bandwidth of difference amplifier ? Explain in detail. 8
3. (A) Explain the frequency response of open loop voltage gain and closed loop voltage gain. 8
(B) Explain the use of Op-Amp as :
(i) Integrator
(ii) Differentiator. 8

OR

- (P) Explain the use of Op-Amp as :
(i) Adder
(ii) Subtractor. 8
(Q) Explain the use of Op-Amp as :
(i) Current voltage convertor
(ii) Voltage to current convertor. 8

4. (A) Explain the following signal filters using Op-Amp :

- (i) Band pass filter
- (ii) Butterworth filter. 8

(B) Explain the following circuit using Op-Amp :

- (i) Comparator
- (ii) Schmitt trigger. 8

OR

(P) Explain the following convertor using Op-Amp :

- (i) Voltage to frequency
- (ii) Frequency to voltage. 8

(Q) Explain the following convertors using Op-Amp .

- (i) A to D convertor (any one)
- (ii) D to A convertor (any one). 8

5. (A) Explain the use of 555 timer IC as :

- (i) Bistable multivibrator
- (ii) Astable multivibrator. 8

(B) Draw the block diagram of 565 phase lock loop IC and explain the function of each block.
State applications of 565 PLL. 8

OR

(P) Draw the block diagram of 555 timer IC and explain the function of various blocks. 8

(Q) Explain the operation of 565 PLL as :

- (i) Fixed voltage regulator
- (ii) Switching regulator. 8