

AM-222

B.C.A Part-I (Semester-I) Examination
DIGITAL TECHNIQUES – 1ST3

Time : Three Hours]

[Maximum Marks : 60

- Note :** (1) **ALL** questions are compulsory.
(2) Draw diagrams wherever necessary.

EITHER

1. (A) What is Logic Gates ? Explain truth table and symbol of NOR and EX-NOR gate. 6
(B) Convert $(26.6)_{10}$ into Binary, Octal and Hexadecimal number system. 6

OR

- (P) Perform the following conversion and find the value of x :
(i) $(2013)_8 \rightarrow (x)_2$
(ii) $(AB.CF)_{16} \rightarrow (x)_8$
(iii) $(111010.0110)_2 \rightarrow (x)_{16}$ 6
(Q) Subtract $(1010)_2$ from $(1101)_2$ using 1's and 2's complement method. 4
(R) Draw the symbol of NAND and EX-OR gate. 2

EITHER

2. (A) What is CMOS logic ? Explain construction and working of two input CMOS NAND gate. 8

(B) Define the terms :

- (i) Fan-in
- (ii) Fan-out
- (iii) Propagation delay
- (iv) Noise immunity. 4

OR

- (P) Draw the circuit diagram of two input TTL NAND gate. Explain its construction and working. 8
- (Q) State the specification and application of DTL NAND gate. 4

EITHER

3. (A) State and prove first and second De-Morgan's theorems using truth table. 6

(B) Simplify the following Boolean equation :

- (i) $y = ABC + \overline{A}BC + A\overline{B}C$
- (ii) $y = ABC + \overline{A}BC + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + \overline{A}BC$. 6

OR

(P) Draw the logic diagram and truth table for Boolean equation $y = A + \overline{A}B + \overline{A}\overline{B}$. 6

(Q) Draw k-map and simplify the following Boolean equation :

$$f(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10). \quad 6$$

EITHER

4. (A) What is Half adder ? Explain the construction and working of half adder. 6

(B) Draw the logic diagram of 4 bit parallel adder. 3

(C) State the difference between half adder and full adder. 3

OR

(P) Explain the construction and working of full subtractor. 6

(Q) Explain the IC 74181 as ALU. 3

(R) Draw the logic diagram of full adder. 3

EITHER

5. (A) What is Demultiplexer ? Explain the construction of 1 : 4 demultiplexer with logic diagram and truth table. 8

(B) Explain use of Decoder as Demultiplexer. 4

OR

(P) What is Decoder ? Explain construction of 2 : 4 decoder with logical diagram and truth table. 8

(Q) State the difference between Multiplexer and Demultiplexer. 4