

**B.Sc. Part-I Semester-I Examination**  
**ELECTRONICS**  
**(Basic Electronics)**

Time : Three Hours]

[Maximum Marks : 80

- N.B.:**— (1) Question No. 1 is compulsory.  
(2) Draw neat diagram wherever necessary.

1. (A) Fill in the blanks :

- (i) KVL stands for \_\_\_\_\_.
- (ii) The unit of resistance is \_\_\_\_\_.
- (iii) SCR stands for \_\_\_\_\_.
- (iv) VLSI stands for \_\_\_\_\_.

2

(B) Choose the correct answer :

- (i) The unit of inductance is \_\_\_\_\_.
  - (a) ohm
  - (b) mho
  - (c) Henry
  - (d) Farad
- (ii) CRT stands for \_\_\_\_\_.
  - (a) Current reactance tube
  - (b) Cathode ray tube
  - (c) Cathode ray transistor
  - (d) None of these
- (iii) PIV indicates \_\_\_\_\_.
  - (a) Peak inverse voltage
  - (b) Positive inverse voltage
  - (c) Peak integrated value
  - (d) None of these
- (iv) IC stands for \_\_\_\_\_.
  - (a) Integrated circuit
  - (b) Ionisation current
  - (c) Inverse current
  - (d) None of these

2

(C) Answer in **one** sentence :

- (i) What is inductor ?
- (ii) What is CRT ?
- (iii) Define Rectification.
- (iv) What is MOSFET ?

4

**EITHER**

- 2. (A) Explain wire wound and carbon composition resistors.
- (B) Explain KVL and KCL.

6

6

**OR**

- (P) Explain the working of transformer.
- (Q) State and prove Thevenin's theorem.

4

8

**EITHER**

- 3. (A) Explain multirange voltmeter.
- (B) Explain multirange ammeter.

6

6

**OR**

(P) Explain CRT with diagram. 7

(Q) Explain working of shunt type ohmmeter. 5

**EITHER**

4. (A) Explain forward biased PN junction diode. 6

(B) Draw the forward V/I characteristics of PN junction diode and explain it. 6

**OR**

(P) Explain construction and working of Half Wave Rectifier Circuit. 6

(Q) Draw the block diagram of regulated power supply and explain function of each block. 6

**EITHER**

5. (A) What is transistor ? Explain PNP transistor. 8

(B) Define  $\alpha$  and  $\beta$  of a transistor. Show the relation between them. 4

**OR**

(P) Draw the circuit of CE amplifier using NPN and PNP transistor. 4

(Q) Explain biasing and stability and Load Line concept. 8

**EITHER**

6. (A) What is FET ? Explain its construction and working. 6

(B) Define FET parameters. Show that  $\mu = r_d \times g_m$ . 6

**OR**

(P) Explain construction, working and characteristics of LDR. 6

(Q) What is photodiode ? Explain its working. 6

**EITHER**

7. (A) State the classification of IC. 4

(B) Explain basic steps in fabrication of monolithic IC. 8

**OR**

(P) Explain scale of integration in IC's. 4

(Q) Explain fabrication of Diode and transistor in monolithic IC. 8