

OR

- (p) Draw logic diagrams and truth table for D, T and RS Flip Flops. 6
- (q) Draw and explain JKMS FlipFlop. 6

EITHER

5. (a) Draw and explain working of Ripple counter with timing diagram. 6
- (b) Explain in detail the 4-bit ring COUNTER. 6

OR

- (p) Draw and explain MOD-10 counter with suitable waveforms 6
- (q) Explain SIPO shift register. 6

EITHER

6. (a) Draw and explain working of decimal to BCD encoder. 6
- (b) Explain 4 : 1 multiplexer in detail. 6

OR

- (p) Draw and explain working of 2 : 4 line decoder. 6
- (q) Explain the 1 : 4 demultiplexer with suitable logic diagram. 6

EITHER

7. (a) Explain different types of Semiconductor memories. 6
- (b) Explain primary and secondary memories with suitable examples. 6

OR

- (p) Explain the concept of memory hierarchy. 6
- (q) Explain volatile and non-volatile memory with example. 6

UBS—50065

4

2750

AQ-663A

B.Sc. (Part-I) Semester-II Examination
2S : ELECTRONICS
(Digital Electronics)

Time : Three Hours]

[Maximum Marks : 80

- Note :-** (i) ALL questions carry equal marks.
(ii) Draw neat sketches wherever necessary.

1. (A) Fill in the blanks :

- (i) A full adder has _____ inputs and two outputs.
- (ii) TTL stands for _____.
- (iii) A demultiplexer has _____ inputs and many outputs.
- (iv) EPROM is _____ ROM. 2

(B) Choose correct alternative and rewrite the following :

- (i) A delay flipflop is also called _____.
- (a) DFF
- (b) JKFF
- (c) TFF
- (d) None

UBS—50065

1

(Contd.)

(ii) If A and B are two inputs to AND gate then its output will be _____.

- (a) A.B
- (b) A+B
- (c) $A \oplus B$
- (d) None

(iii) The radix of an octal number system is _____.

- (a) 2
- (b) 4
- (c) 8
- (d) 16

(iv) A MOD - 5 counter can count up to _____ clock pulses.

- (a) 08
- (b) 05
- (c) 07
- (d) None.

2

(C) Answer the following in **one** sentence :

- (i) What is monostable multivibrator ? 1
- (ii) What is shift register ? 1
- (iii) What is a multiplexer ? 1
- (iv) What does pair stand for in K-map ? 1

EITHER

2. (a) Give the logic symbols, boolean equation and truth table for OR and NOR gates. 6
- (b) Explain construction and working of G-bit binary adder. 6

OR

- (p) Convert $(30.6)_{10}$ to binary, octal and hexadecimal number system. 6
- (q) Give the logic symbols, boolean equation and truth table for NAND and Ex-OR gates. 6

EITHER

3. (a) Explain Fan-in, Fan-out and noise immunity related to digital IC's 6

(b) Prove :

$$(i) (A+B)(A+C) = A + BC$$

$$(ii) (A + B) (\bar{A} + C) = AC + \bar{A} B \quad 6$$

OR

- (p) State and prove the De Morgan's theorem. 6
- (q) Draw and explain the working of TTL NAND gate. 6

EITHER

4. (a) Draw and explain the working of JKFF with truth table. 6
- (b) Explain transistorized monostable multivibrator. 6