

B.Sc. (Part-I) Semester-II Examination
ELECTRONICS
(Digital Electronics)

Time : Three Hours]

[Maximum Marks : 80

- N.B.** :- (1) All questions carry equal marks.
(2) Draw neat sketches wherever necessary.

1. (A) Fill in the blanks :

- (i) CMOS stands for _____.
- (ii) A half adder has _____ outputs.
- (iii) The base of a number system is also called as _____.
- (iv) MOD-5 counter requires _____ no. of flip-flops. 2

(B) Choose correct alternative & rewrite the following :

- (i) PROM is _____ memory.
 - (a) Programmable
 - (b) Read only
 - (c) Programmable read only
 - (d) None
- (ii) To avoid race around condition _____ flip flop is used.
 - (a) RS
 - (b) JK
 - (c) JKMS
 - (d) none
- (iii) The base of octal number system is :
 - (a) 2
 - (b) 4
 - (c) 8
 - (d) 16
- (iv) 1's complement of 0101 is :
 - (a) 1111
 - (b) 1100
 - (c) 1010
 - (d) None 2

(C) Answer in **one** sentence :

- (i) What is encoder ?
- (ii) What is Astable Multivibrator ?
- (iii) What is Demultiplexer ?
- (iv) What is ROM ?

4

EITHER

2. (a) Convert the following :

(i) $(1110.11)_2 = (x)_{10}$

(ii) $(031.1)_8 = (x)_{10}$

(iii) $(03FF)_{16} = (x)_{10}$

6

(b) Give logic symbols, boolean equations and truth table for NOT, OR and NOR gates. 6

OR

(p) Explain construction and working of 4-bit adder. 6

(q) Explain EX-OR and EX-NOR gates with truth table and give the logic equations of both the gates. 6

EITHER

3. (a) Explain any three characteristics of Logic Families. 6

(b) Prove that :

(i) $\overline{(\overline{A + B})} = \overline{A} \cdot \overline{B}$

(ii) $\overline{(\overline{A \cdot B})} = \overline{A} + \overline{B}$

6

OR

(p) Explain TTL NAND gate with suitable diagram. 6

(q) Explain the various types of grouping used in K.maps to reduce the logic gates. 6

EITHER

4. (a) Draw the logic diagram of RS-flip flop and explain its working. Draw truth table. 6

(b) Draw and explain construction and working of transistorized monostable multivibrator. 6

OR

(p) Draw and explain JKMS flip-flop. 6

(q) Explain JKFF. What is race around condition ? 6

EITHER

5. (a) Explain the working of SISO shift register. 6
 (b) Explain the working of ring counter with truth table. 6

OR

- (p) Explain working of asynchronous up counter with suitable diagram and waveform. 6
 (q) Explain SIPO shift register with truth table. 6

EITHER

6. (a) Explain 1 : 4 demultiplexer in detail. 6
 (b) Draw and explain decimal to BCD encoder with suitable diagram. 6

OR

- (p) Explain operation of BCD to decimal decoder. 6
 (q) Explain operation of 4 : 1 multiplexer. 6

EITHER

7. (a) State types of semiconductor memories. Explain any two types. 6
 (b) Explain the concept of memory Hierarchy. 6

OR

- (p) Explain primary and secondary memories. 6
 (q) Explain volatile and non-volatile memories. 6

