

**B.Sc. (Part-I) Semester-II Examination****2S : ELECTRONICS****(Digital Electronics)**

Time : Three Hours]

[Maximum Marks : 80

**N.B. :—** (1) All questions are compulsory.

(2) Draw neat sketches wherever necessary.

1. (A) Fill in the blanks :

(i) The Boolean equation of AND gate is  $y = \underline{\hspace{2cm}}$ . ½(ii) The Base of Decimal number system is  $\underline{\hspace{2cm}}$ . ½(iii) PIPO is parallel in  $\underline{\hspace{2cm}}$  out shift Register. ½(iv) EPROM stands for  $\underline{\hspace{2cm}}$  Programmable Read Only Memory. ½

(B) Choose correct alternative and rewrite the following :

(i) 1's complement of 0011 is :

(a) 1111 (b) 1101(c) 1110 (d) 1100 ½

(ii) The Boolean equation of OR gate is :

(a)  $A+B$  (b)  $A.B$ (c)  $\overline{A.B}$  (d)  $\overline{A+B}$  ½(iii) RAM and ROM are called  $\underline{\hspace{2cm}}$ .(a) Semi conductor memory (b) Auxiliary memory(c) Magnetic memory (d) None of the above ½

(iv) In D flip flop D stands for \_\_\_\_\_.

- (a) Diode (b) Dual  
(c) Delay (d) None

½

(C) Answer in **one** sentence :

- (i) State different types of flip flops. 1  
(ii) What is multiplexer ? 1  
(iii) What is counter ? 1  
(iv) What is Base of a Number System ? 1

**EITHER**

2. (A) Perform the following conversions :

(i)  $(11001)_2 = (x)_{10}$

(ii)  $(1010.101)_2 = (x)_{10}$

(iii)  $(32)_{10} = (x)_2$

6

(B) Give logic symbol, Boolean equation and truth table of NOT, AND, OR gates.

6

**OR**

(P) Explain the working of 4-Bit Binary adder.

6

(Q) Draw a logic symbol, Boolean equation and truth table of XOR gate. Explain its working.

6

**EITHER**

3. (A) State and prove De' Morgan's Theorems.

6

(B) Explain the working of CMOS NAND gate.

6

**OR**

(P) What is K-map ? Draw a K-map for 2, 3 and 4 input variables.

6

(Q) Explain the working of DTL NAND gate.

6

**EITHER**

4. (A) Draw the circuit diagram of clocked RS flip flop and explain its working.

6

(B) Draw a neat circuit diagram of Astable multivibrator and explain its working.

6

**OR**

- (P) Explain construction and working of monostable multivibrator. 6
- (Q) Explain the working of JK flip flop with truth table. 6

**EITHER**

5. (A) Explain the working of Ring counter. 6
- (B) What is Shift Register ? Explain working of SISO Shift Register. 6

**OR**

- (P) Explain the working of 4-Bit Ripple counter. 6
- (Q) Explain PIPO Shift Register. 6

**EITHER**

6. (A) Draw a neat circuit diagram of 4:1 multiplexer and explain its working. 6
- (B) Explain the working of BCD to decimal decoder. 6

**OR**

- (P) Explain the working of 1:4 Demultiplexer. 6
- (Q) Explain the working of decimal to BCD Encoder. 6

**EITHER**

7. (A) Explain primary and secondary memories with suitable examples. 6
- (B) Explain the concept of memory Hierarchy. 6

**OR**

- (P) What are different types of magnetic memories ? State its advantages and disadvantages. 6
- (Q) What is volatile and non-volatile memory ? Give examples of each. 6

