

OR

- (P) Explain any three characteristics of logic families. 6
- (Q) State any three boolean laws. 3
- (R) Draw k maps for 2, 3 and 4 variables for fundamental products terms. 3

EITHER

4. (A) Explain the working of D-flip flop. 6
- (B) Explain working of Astable multivibrator. 6

OR

- (P) Explain working of Monostable Multivibrator. 6
- (Q) Explain working of JK flip flop. 6

EITHER

5. (A) Explain the working of Ring Counter with neat diagram. 6
- (B) Explain SISO Shift Register. 6

AR - 523

4

AR - 523

Second Semester B. Sc. (Part - I) Examination

2S - ELECTRONICS

Digital Electronics

P. Pages : 6

Time : Three Hours]

[Max. Marks : 80

- Note :** (1) All questions are compulsory.
(2) Draw neat diagram wherever necessary.

1. (A) Fill in the blanks.

(i) The 1's' compliment of 010 is _____.

$\frac{1}{2}$

(ii) According to De Morgan's Theorem $A+B$ is equals to _____.

$\frac{1}{2}$

(iii) Flip flop is a _____ multivibrator.

$\frac{1}{2}$

(iv) PIPO is a parallel in _____ out shift register.

$\frac{1}{2}$

(B) Choose correct alternative and rewrite the sentence.

(i) The base of Hexadecimal number system is

(a) 2 (b) 10

(c) 8 (d) 16

$\frac{1}{2}$

AR-523

P.T.O.

(ii) The boolean equation for NOT gate is

- (a) $y = A$ (b) $y = \overline{\overline{A}}$
 (c) $y = \overline{A}$ (d) $y = AA$ $\frac{1}{2}$

(iii) In D flip flop when CLK=1 and D=1 then output of flip flop is

- (a) 1 (b) 0
 (c) Toggle (d) None of above $\frac{1}{2}$

(iv) Asynchronous counters are also called as

- (a) Parallel (b) Ripple
 (c) Dual (d) Johnson counter $\frac{1}{2}$

(C) Answer the following in **one** sentence.

- (i) State different types of Basic logic gates. 1
 (ii) State types of shift registers. 1
 (iii) State types of ROM. 1
 (iv) State different types of flip flops. 1

EITHER

2. (A) Perform the following conversion.

(i) $(25)_{10} = (x)_8$

(ii) $(10100)_2 = (x)_{10}$

(iii) $(12.25)_{10} = (x)_2$ 6

(B) Explain the working of Half Adder. 4

(C) What is 1's' compliment ? Give example. 2

OR

(P) Define NAND and NOR gates and draw truth tables and symbols. 6

(Q) Explain Excess-3 and BCD-8421 codes. 4

(R) Perform the following :—

(i) $(101)_2 \times (100)_2$

(ii) $(1100)_2 + (0011)_2$ 2

EITHER

3. (A) State and prove De Morgan's theorems. 6

(B) Give the classification of logic families and explain the working of TTL logic (NAND) gate. 6

OR

- (P) Explain working of Johnson counter. 6
(Q) Explain PIPO shift register. 6

EITHER

6. (A) Explain the working of 4:1 multiplexer. 6
(B) Explain the working of BCD to seven segment decoder. 6

OR

- (P) Explain the working of 1:4 Demultiplexer. 6
(Q) Differentiate between multiplexer and Demultiplexer. 4
(R) What is decoder ? 2

EITHER

7. (A) Explain primary and secondary memories. 6
(B) Explain the concept of memory Hierarchy. 6

OR

- (P) Explain different types of semiconductor memories. 6
- (Q) Differentiate between volatile and Non volatile memory. 4
- (R) What is primary and secondary memory ? 2

