

**B.Sc. Part-II (Semester-III) Examination**  
**ELECTRONICS**  
**(Electronics Devices and Circuits)**

Time : Three Hours]

[Maximum Marks : 80

**Note** :— (1) Question No. 1 is compulsory.

(2) Draw neat diagrams wherever necessary.

1. (A) Fill in the blanks with correct word : 2

(i) In ideal Op-Amp value of input impedance is \_\_\_\_\_.

(ii) Bistable multivibrator has \_\_\_\_\_ stable states.

(iii) D/A is known as \_\_\_\_\_.

(iv) Voltage gain of Non-inverting amplifier is \_\_\_\_\_.

(B) Choose the correct alternative : 2

(i) In ideal Op-Amp bandwidth is :

(a) Zero

(b) Minimum

(c) Infinite

(d) None

(ii) The monostable multivibrator has \_\_\_\_\_ stable state(s).

(a) 2

(b) 1

(c) 3

(d) 4

(iii) One of the following is not an oscillator :

(a) Colpitts

(b) Wein bridge

(c) Push pull

(d) Hartley

(iv) Op-Amp IC 741 has total \_\_\_\_\_ pins.

(a) 2

(b) 6

(c) 14

(d) 8

(C) Answer the following questions in **ONE** sentence : 4

(i) What is feedback ?

(ii) List the hybrid parameters.

(iii) Define CMRR.

(iv) What is oscillator ?

**EITHER**

2. (A) Give the advantages and disadvantages of direct coupled amplifier. 4

(B) Draw hybrid equivalent circuit for CE transistor amplifier and derive the expression for

(i) Current gain, (ii) Input impedance for CE-transistor amplifier. 8

**OR**

(P) Explain the working of single tuned amplifier with circuit diagram. 8

(Q) State the advantages and disadvantages of RC coupled amplifier. 4

**EITHER**

3. (A) Explain the construction and working of Class B push pull amplifier. Find its efficiency. 8  
(B) Explain cross over distortion. How it is eliminated ? 4

**OR**

- (P) Draw a circuit diagram of transformer coupled Class A amplifier and derive expression for its efficiency. 8  
(Q) Give the classification of amplifiers. 4

**EITHER**

4. (A) Explain Barkhausen criterion for sustained oscillations. 4  
(B) Explain the construction and working of Hartley oscillator. 8

**OR**

- (P) Explain the construction and operation of RC-phase shift oscillator using transistor. State its advantages. 8  
(Q) State the advantages of negative feedback. 4

**EITHER**

5. (A) Explain the working of Op-Amp as non-inverting amplifier and derive the expression for voltage gain. 6  
(B) With suitable diagram explain the working of Op-Amp as summing amplifier. 6

**OR**

- (P) Explain the concept of virtual ground in Op-Amp. 4  
(Q) Define : 2  
(i) Common mode voltage gain  
(ii) Differential mode voltage gain.  
(R) Draw the block diagram of Op-Amp and explain the function of each block. 6

**EITHER**

6. (A) Explain the construction and working of Op-Amp as a monostable multivibrator. 6  
(B) Explain how Op-Amp is used as damped harmonic oscillator. 6

**OR**

- (P) Explain the working of Op-Amp as a Schmitt Trigger. 6  
(Q) Explain the working of Op-Amp as an astable multivibrator. 6

**EITHER**

7. (A) Explain the working of successive approximation type A/D converter. 8  
(B) Explain the terms :  
(i) D/A Accuracy  
(ii) D/A Resolution. 4

**OR**

- (P) Describe the construction and working of Weighted Resistor type D/A Converter. 6  
(Q) Explain the need of D/A and A/D converter. 4  
(R) What is A/D and D/A converter ? 2