

B.Sc. (Part-II) Semester—III Examination
3S : ELECTRONICS
(Electronic Devices and Circuits)

Time : Three Hours]

[Maximum Marks : 80

Note :—(1) Q.No. 1 is compulsory.

(2) Draw neat diagram wherever necessary.

1. (A) Fill in the blanks with correct word :— $\frac{1}{2} \times 4 = 2$
- (i) For a transistor number of h-parameters are _____.
 - (ii) The voltage gain of non inverting Op-Amp is _____.
 - (iii) In phase-shift oscillator each RC combination gives _____ degree phase shift.
 - (iv) The CMRR of an ideal difference amplifier is _____.
- (B) Choose correct alternative and rewrite the answer :— $\frac{1}{2} \times 4 = 2$
- (i) Cross over distortion occur in _____ amplifier :
 - (a) Push pull
 - (b) Class A
 - (c) Class B
 - (d) Class AB
 - (ii) The monostable multivibrator has one stable and another one as a _____ State.
 - (a) Stable
 - (b) Quasistable
 - (c) Unstable
 - (d) None
 - (iii) The D/A convertor converts digital signal into _____ signal.
 - (a) Square wave
 - (b) Sine
 - (c) Digital
 - (d) Analog
 - (iv) Op-Amp IC 741 has total _____ Pins.
 - (a) 2
 - (b) 6
 - (c) 14
 - (d) 8

(C) Answer the following questions each in one sentence only :— 1×4=4

- (1) State Barkhausen criteria for oscillator.
- (2) State any one ideal parameter of Op-Amp.
- (3) Give any one advantage of negative feedback.
- (4) Define Band Width in case of RC-coupled amplifier.

EITHER

2. (A) Explain working of RC-coupled amplifier with circuit diagram and frequency response. 8
- (B) Explain the terms :—
 - (i) Lower cut off frequency
 - (ii) Upper cut off frequency. 4

OR

- (P) Give the advantages and disadvantages of direct coupled amplifier. 4
- (Q) Draw circuit diagram of CE amplifier and obtain its hybrid equivalent circuit. Also derive expression for — (i) Output Impedance, (ii) Input Impedance. 8

EITHER

3. (A) Explain construction and working of Complementary Symmetry Class-B push-pull amplifier. 8
- (B) Explain cross over distortion. How it is eliminated? 4

OR

- (P) Draw and explain a circuit diagram of transformer coupled Class-A amplifier and derive expression for its efficiency. 8
- (Q) Explain classification of amplifier based on biasing condition. 4

EITHER

4. (A) State the difference between amplifier and oscillator. 2
- (B) Explain construction and working of colpitts oscillator. 6
- (C) Explain the effect of negative feedback on bandwidth. 4

OR

- (P) Explain construction and working of Wein bridge oscillator. 6
- (Q) Draw a circuit diagram of RC-phase shift oscillator and explain its working. 6

EITHER

5. (A) Explain the concept of Virtual ground. 4
 (B) Explain the working of Op-Amp as an integrator. 4
 (C) Explain working of Op-Amp as inverting amplifier. 4

OR

- (P) Explain working of a difference amplifier. 6
 (Q) Draw block diagram of IC Op-Amp and explain function of each block. 6

EITHER

6. (A) Explain the working of Op-Amp as an astable multivibrator. 6
 (B) Explain Op-Amp as a regenerative comparator with circuit diagram and waveforms. 6

OR

- (P) Explain working of Op-Amp as logarithmic amplifier. 6
 (Q) Explain how Op-Amp is used as damped harmonic oscillator, write necessary steps. 6

EITHER

7. (A) Describe the successive-approximation type A/D converter. 6
 (B) Explain the terms :—
 (i) Accuracy
 (ii) Resolution
 (iii) Linearity in D/A converter. 6

OR

- (P) Explain the action of weighted ladder type D/A converter. 6
 (Q) Explain need of A/D and D/A converter. 6

