

AR - 548

Third Semester B.Sc. (Part - II) Examination

**3S: ELECTRONICS**

(Electronics Devices and Circuits)

P. Pages : 7

Time : Three Hours ]

[Max. Marks : 80

---

- Note :** (1) Question No. **One** is compulsory.  
(2) Draw neat diagram wherevve necessary.

1. (A) Fill in the blanks with correct word :—
- (i) Voltage gain of emitter follower is nearly  
——
  - (ii) The conduction angle of class B amplifier  
is —— degree.
  - (iii) In ideal op-Amp value of input  
impedance is ——
  - (iv) A Bistable multivibrator has —— stable  
state.  $\frac{1}{2} \times 4 = 2$
- (B) Choose correct alternative and rewrite the  
answer :—
- (i) The h-parameters are called hybrid

AR-548

P.T.O.

because they —

- (a) Obtained from different characteristics.
- (b) Are mixed with units
- (c) Are added with other parameters
- (d) None

(ii) Multistage amplifiers are used in order to achieve —

- (a) Voltage amplification.
- (b) Power gain.
- (c) Frequency response.
- (d) All of the above.

(iii) One of the following is not an oscillator —

- (a) Colpitts
- (b) Wein bridge
- (c) Push pull
- (d) Hartley.

(iv) R-2R ladder circuit used to convert —

- (a) Digital to analog
- (b) Analog to digital

(c) Sine to square wave

(d) None.

$$\frac{1}{2} \times 4 = 2$$

(C) Answer the following question in **one** sentence

(i) List the hybrid parameters.

(ii) Give the basic criteria for oscillator.

(iii) Define CMRR.

(iv) Efficiency of class-A transformer coupled power amplifier is ?  $1 \times 4 = 4$

**EITHER**

2. (A) Explain cascaded amplifier with various types of coupling. 4

(B) Explain working of single tuned amplifier with circuit diagram. 8

**OR**

(P) Define h-parameter of CE-configuration. 4

(Q) Draw equivalent hybrid circuit for CE transistor amplifier. Derive the expression for (i) current gain (ii) Input impedance for a single stage CE-transistor amplifier. 8

**EITHER**

3. (A) Explain construction and working of class-B. Push pull amplifier. Derive the equation for its efficiency. 8
- (B) State advantages and disadvantages of class-B push pull power amplifier. 4

**OR**

- (P) State the difference between voltage amplifier and power amplifier. 4
- (Q) Explain construction and working of transformer coupled class A amplifier. Show the efficiency of transformer coupled resistive load class-A power amplifier is 50%. 8

**EITHER**

4. (A) What is oscillator ? Explain Barkhausen criterion of oscillations. 4
- (B) Explain construction and working of phase shift oscillator using transistor. 8

**OR**

- (P) State the advantages and disadvantages of negative feed back. 4

- (Q) Explain the effect of negative feed back on stability of an amplifier gain. 4
- (R) Draw the block diagram for the following.
- (i) Voltage series feed back.
- (ii) Current shunt feed back. 4

**EITHER**

5. (A) State parameters of ideal Op-Amp. 2
- (B) Explain the terms :—
- (i) CMRR.
- (ii) Slew Rate.
- (iii) Open loop gain. 6
- (C) Explain the working of Op-Amp as differentiator. 4

**OR**

- (P) Explain the working of Op-Amp as non – inverting amplifier. 4
- (Q) Explain the working of Op-Amp as subtractor. 4

- (R) What is difference amplifier ? State its advantages. 4

**EITHER**

6. (A) Draw neat diagram and explain the operation of Op-Amp as a monostable multivibrator. 6

- (B) Show a possible computer set up required for solving following simultaneous equation

$$5x + 2y = 1 \text{ --- } \textcircled{1}$$

and  $3x - 6y - 2 = 0 \text{ --- } \textcircled{2}$  6

**OR**

- (P) Explain how Op-Amp can be used as an astable multivibrator. Derive expression for the frequency of multivibrator. 6

- (Q) Explain the working of Op-Amp as a logarithmic amplifier. 6

**EITHER**

7. (A) Explain the working of R-2R ladder type A/D converter. 6

- (B) Draw block diagram of counter type A/D converter and explain its operation with timing diagram. 6

**OR**

- (P) Explain the working of successive approximation A/D converter. 6
- (Q) Draw block diagram of single slope A/D converter and explain its working. 6



