

M.E. First Semester (Electrical (Electronics & Power) Engg.) (New-CGS)

13314 : Power Electronic Converters : 1 EEPME 2

P. Pages : 1

Time : Three Hours



AW - 3849

Max. Marks : 80

- Notes :
1. Answer **three** question from Section A and **three** question from Section B.
 2. Due credit will be given to neatness and adequate dimensions.
 3. Assume suitable data wherever necessary.
 4. Use of pen Black ink/refill only for writing the answer book.

SECTION - A

1. a) Explain series and parallel operations of thyristors. 7
b) Explain the working principle of IGBT in brief. 7

OR

2. a) Explain switching principle of GTO. 7
b) What is power MOSFET ? Explain its switching principles. 7

3. a) Explain the operating principles of DC-DC converter. 7
b) What is Buck Principle ? Explain it with respect to converters. 6

OR

4. a) Explain the operating phenomenon of SEPIC converter. 7
b) Explain the operating principle of flyback converters. 6

5. Explain the detail design procedure of Transformer. 13

OR

6. a) What do you mean by Electrical characteristics of Transformer ? Explain in brief. 7
b) How to design an Inductor ? Explain in brief. 6

SECTION - B

7. For 3ϕ inverter can you elaborate the 120° modes of operation. 14

OR

8. For an 3ϕ inverter can you illustrate its 180° mode of operation. 14

9. Discuss in detail how chopper can act as a DC base drive assembly. 13

OR

10. What are the different types of single phase converters, single phase drive ? Explain in brief. 13

11. a) How PWM techniques are used for AC controllers ? Discuss. 6
b) For cycloconverters, explain how phase of O/P is controlled. 7

OR

12. Discuss the principle of cycloconverter with the effect of circulating and non-circulating current. 13
