

M.E. Second Semester (Electrical & Elect.) (New-CGS)  
**13293 : Elective-II : Flexible AC Transmission Systems : 2 EEEME 5**

P. Pages : 2

Time : Three Hours



**AW - 3846**

Max. Marks : 80

- Notes :
1. Answer **three** question from Section A and **three** question from Section B.
  2. Assume suitable data wherever necessary.
  3. Use of pen Blue/Black ink/refill only for writing the answer book.

**SECTION - A**

1. a) What is importance of Reactive power in transmission line? Explain basic principle of power flow in transmission line with simplified model and phasor diagram. 7  
b) Explain Surge Impedance and Ferranti Effect of transmission line. 6

**OR**

2. a) Explain necessity of reactive power compensation in transmission line. 6  
b) What are the conventional reactive power compensation mechanisms Explain Any two methods for conventional reactive power compensation. 7
3. a) What is SVC? Explain objective of SVC, Shunt compensator. Draw and explain the circuit element diagram of SVC (TCR+FC) also state operating V-I area of (TCR+FC) SVC type var generator. 7  
b) Explain effect of variation of firing angle  $\alpha$  on fundamental reactor current. 7

**OR**

4. a) Explain fixed capacitor, Thyristor-controlled reactor type Var generator and its var demand versus var output characteristics. 7  
b) Give comparison of var generators 7  
i) TCR-FC and ii) TSC (TSR)
5. a) Draw and Explain V-I and V-Q characteristics of STATCOM and SVC also compare the operating zones. 7  
b) With the help of Block diagram Explain transient stability enhancement with SVC. 6

**OR**

6. a) Explain power oscillation damping and How it is implemented with SVC and STATCOM. 7  
b) Draw and explain transmitted power versus transmission angle of a two machine system with a midpoint SVC obtained with different var ratings. 6

## SECTION - B

7. a) What is meant by TCSC, Write down the expression for equivalent impedance, capacitive and inductive reactance of TCSC also, give the different modes of operation of TCSC. 8
- b) Explain the locations to place TCSC in a power system. 6

OR

8. a) Derive and explain the series compensation of symmetrical line. 7
- b) Explain the effect of TCSC for enhancement of system damping. 7
9. a) What is voltage source converter Draw and explain reactive power compensation with help of shunt compensator STATCOM, also explain how active and reactive power can be control with the STATCOM. 13

OR

10. a) What is Static Synchronous Series Compensator (SSSC) Draw and explain its working operation and different operating modes also state applications of SSSC. 13
11. a) Derive the expression of UPFC connected at midpoint. 8
- b) Give the block diagram for a basic UPFC control scheme. 5

OR

12. a) Explain in detail with analysis about the implementation of UPFC using back to back connected VSC with common DC link. 13

\*\*\*\*\*