

M.E. Second Semester (Electrical & Elect.) (New-CGS)  
**13293 : Elective-II : Flexible AC Transmission Systems**  
**2 EEEME 5**

P. Pages : 2  
Time : Three Hours



**AW - 3575**  
Max. Marks : 80

- Notes : 1. Answer **three** question from Section A and **three** question from Section B.  
2. Assume suitable data wherever necessary.  
3. Use of pen Blue/Black ink/refill only for writing the answer book.

**SECTION - A**

1. a) Why a flexible AC transmission system required ? Explain the reactive power compensation of transmission line. 7  
b) State and explain the objective of series and shunt compensation of transmission line. 7

**OR**

2. a) What is reactive power compensation. Explain working of conventional reactive power compensators. 7  
b) Explain power flow control of transmission line with simple two machine system, with active and reactive power flow phasor diagram and power angle curve for different values of X. 7  
3. a) Draw V-I characteristics of SVC and explain its operating modes. 6  
b) Explain applications of SVC also state general advantages of SVC. 7

**OR**

4. a) How the effective admittance BL varies by firing angle control of SVC ? Explain with the help of basic structure of SVC (TCR&FC) and susceptance vs firing angle plot of SVC and waveforms of SVC. 13  
5. a) Draw and explain V-I and V-Q characteristics of SVC and STATCOM. 6  
b) What is transient stability ? Explain improvement of transient stability with midpoint SVC. 7

**OR**

6. a) Explain merits of hybride compensator. 6  
b) Explain how power oscillation damping and subsynchronous damping can be achieved with SVC. 7

**SECTION - B**

7. a) What is TCSC ? Explain its working with basic circuit elements. 7  
b) Draw and explain the variation of TCSC reactance with firing angle  $\alpha$ . 6

**OR**

8. a) Explain improvement of system stability using TCSC. 7  
b) State and explain advantages of TCSC. 6  
9. a) Give construction and working of VSC based shunt compensator with its V-I characteristics. 7  
b) Explain voltage regulation mode and Var control mode of operation of STATCOM. 7

**OR**

10. a) Explain the working of STATCOM compare its performance with SVC. 7  
b) Compare STATCOM and SSSC voltage source based shunt and series controller. 7  
11. a) Draw and explain working of UPFC by two back to back voltage sourced converters. 7  
b) Explain independent real and reactive power flow control using UPFC of two machine system. 6

**OR**

12. a) Explain functional control of shunt converter and series converter in UPFC. 7  
b) Give details about basic control system for P and Q control for series and shunt converter. 6

\*\*\*\*\*