

M.E. Second Semester (Electrical Engineering (Electrical Power System))
Application of Power Electronics to Power System
EP 2205

P. Pages : 2

Time : Three Hours



AU - 3429

Max. Marks : 80

- Notes :
1. Due credit will be given to neatness and adequate dimensions.
 2. Assume suitable data wherever necessary.
 3. Illustrate your answer necessary with the help of neat sketches.

SECTION – A

1. a) Explain Discrete passive compensation. 7
- b) Explain compensation by a series capacitor connected at the midpoint of line with pure series compensation at the midpoint. 7

OR

2. Draw power angle curve with STATCOM and explain compensation by STATCOM at midpoint of the line. 14
3. a) Explain steady state problem in alternating current system. 4
- b) Analyze the transmission line with SVC connected at midpoint. 9

OR

4. a) Explain in details TSC-TCR. http://www.sgbauonline.com 7
- b) Explain TCSC for stability study with Block diagram. 6
5. a) Explain in brief principle of operation of STATCOM. 7
- b) Compare variable series compensation with SSSC. 6

OR

6. Give the analysis of three phase six pulse STATCOM. 13

SECTION – B

7. a) Describe equivalent ckt of FACTS controller. 7
- b) What are the various PQ problems produces on distribution power system. 7

OR

8. a) Explain Modelling of harmonic propagation. 7
- b) Explain current harmonics generated by thyristor controlled reactors. 7

9. a) What are the various mitigation devices used to minimized the effect of harmonics. 7
b) Explain the working of VSC based series connected active filter. 6

OR

10. a) Explain in brief the effect of resonance. 7
b) Explain different types of harmonics creating loads. 6
11. a) List out the various application of UPFC on the power system. 7
b) How power quality problems can be minimized using power electronic conditioners. 6

OR

12. a) Explain the modeling of UPFC with its equivalent ckt. 7
b) Write the various IEEE power quality standards. 6
