

AQ - 2789

First Semester M. E. (Digital Electronics) (CGS) Examination

MODERN ELECTRONIC DESIGN TECHNIQUES

Paper - 1 UMEF 3

P. Pages : 3

[Max. Marks : 80]

Time : Three Hours]

- Note :** (1) Separate answer book must be used for each section in the subject Geology, Engineering material of civil branch and Separate answer-book must be used for Section A and B in Pharmacy and Cosmetic Tech.
- (2) Answer **Three** questions from Section A and **Three** questions from Section B.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answer wherever necessary with the help of neat sketches.
- (5) Use pen of Blue/Black ink/refill only for writing the answer book.

SECTION A

1. (a) Explain working of PGA AD526. Hence design PGA with gain of 1, 2, 4, 8 and 16. 7
- (b) Explain high speed logic isolators, with the working specifications, hence explain practical application of digital isolation in data acquisition systems. 6

OR

2. (a) Explain digital isolation techniques, hence AD 260/AD 261 High speed logic isolators. 6
- (b) What is i-coupler technology ? Hence explain with specifications the construction of ADuM1100 single channel digital isolator. 7
3. (a) Explain construction of modern Schottky diodes with specifications used in switched mode supplies. 7
- (b) Explain construction and selection of Bipolar transistor, Also passivation on Bipolar transistor. 7

AQ-2789

P.T.O.

OR

4. (a) What is switch mode power converters ? Explain working of buck regulator with waveforms and its design concepts. 8
- (b) Design Boost regulator for $V_{dc} = 20 \text{ V}$ and $V_o = 80 \text{ V}$ with $R_L = 500 \Omega$ and peak to peak ripple voltage = 12 mV, and switching frequency of 12 KHz. 6
5. (a) Explain the working with block diagram of simple coherent pulsed radar. 6
- (b) What is phase lock loop? Explain with block diagram the working of PLL. 7

OR

6. (a) Draw and explain the block diagram of moving target detector system. 6
- (b) Explain working of radar with basic radar range equations. 7

SECTION B

7. (a) Draw and explain electrical starting system of turbine engine starter circuit of aircraft. 6
- (b) Explain engine speed tachometer system and engine temperature monitor system for aircraft. 7

OR

8. (a) Explain various basic flight instruments. 6
- (b) Draw and explain digital engine control system for automobile. 7
9. (a) Explain with block diagram the function of Glucose meter. 7
- (b) Draw and explain a block diagram of non -invasive device for measuring the oxygen content in the blood. 6

OR

10. (a) Explain with block diagram the working of barcode scanner. 7

- (b) Explain with applications the working of ultrasound meters. 6
11. (a) What is thermal management? Draw and explain electrical analog model for heat transfer from component to ambient. Also explain some practices that will improve thermal performance. 8
- (b) Explain rules for design of enclosure for electronic product for EMC, hence explain shielding efficiency. 8

OR

12. (a) What is reliability ? Explain the following design aspect for reliability. MTBF, failure rate, availability, the cost of reliability, simplicity and redundancy. 8
- (b) Explain testability techniques, hence explain In-circuit testing, functional testing by ATE and boundary scan JTAG. 8



